

## Mid-term exam of Electronics

*Calculator and documents are not allowed. The number of points per question is indicative.*

**Answers to be written on this document only. If you need more space, you can use the back of the sheets.**

### Exercise 1. Lecture questions (5 points – without negative points)

Choose the correct answers :

We consider a sinusoidal current  $i(t) = I\sqrt{2} \cdot \sin(\omega t + \varphi)$

1. By convention,  $I$  is any real quantity in Ampere.

a. True

b. False

2. Choose the correct formula.  $T$  represents the period of  $i(t)$  and  $f$  its frequency.

a.  $\omega = 2 \cdot \pi \cdot T$

c.  $f = 2 \cdot \pi \cdot \omega$

b.  $\omega \cdot T = 2 \cdot \pi$

d.  $\frac{\omega}{T} = \frac{2 \cdot \pi}{f}$

We note  $\underline{I}$  the complex amplitude of  $i(t)$ .

3. What is the modulus of  $\underline{I}$  ?

a.  $< i >$

c.  $2 \cdot I$

b.  $I$

d.  $I \cdot \sqrt{2}$

4. What is the argument of  $\underline{I}$  ?

a.  $\omega t + \varphi$

c.  $\omega t$

b.  $\varphi$

d.  $I$

5. Which formula represents the complex impedance of a capacitor  $C$ ?

a.  $-jC\omega$

b.  $\frac{-1}{jC\omega}$

c.  $\frac{1}{jC}$

d.  $\frac{-j}{C\omega}$

6. For a capacitor, the voltage is :

a. In advance of  $\frac{\pi}{2}$   
compared to the  
current

b. Delayed of  $\frac{\pi}{2}$   
compared to the  
current

c. In phase with the  
current

7.  $\frac{1}{C\omega}$  is homogeneous to :

a.  $\Omega$

c.  $s$

b.  $S$

d. Without unit

8. Which formula represents the complex impedance of an inductor  $L$ ?

a.  $jL$

b.  $\frac{1}{jL\omega}$

c.  $jL\omega$

d.  $\frac{-j}{L\omega}$

9. For an inductor, the current is :

a. In advance of  $\frac{\pi}{2}$  compared to the voltage.

b. Delayed of  $\frac{\pi}{2}$  compared to the voltage.

c. In phase with the voltage.

10. What is the unit of  $LC\omega^2$  ?

a.  $\Omega$

c.  $s$

b.  $S$

d. Without unit

### Exercise 2. Identification of a two-terminal circuits (3 points)

We want to determine the type of the unknown two-terminal. For that, we measure the voltage across its terminals  $u(t)$  and the current  $i(t)$  flowing through it.

Determine the type of the two-terminal and its characteristic value ( the value of  $R$  for a resistor, the value of  $C$  for a capacitor and the value of  $L$  for an inductor) for each following case : (justify your answer)


$$1. \quad u(t) = U_{Max} \cdot \sin(\omega t) \text{ and } i(t) = I_{Max} \cdot \sin\left(\omega t - \frac{\pi}{2}\right) \text{ where } \begin{cases} \omega = 1000 \text{ rad/s} \\ U_{Max} = 10 \text{ V} \\ I_{Max} = 10 \cdot 10^{-3} \text{ A} \end{cases}$$

2.  $u(t) = U_{Max} \sin(\omega t)$  and  $i(t) = I_{Max} \cos\left(\omega t - \frac{\pi}{2}\right)$  where  $\begin{cases} \omega = 1000 \text{ rd/s} \\ U_{Max} = 10 \text{ V} \\ I_{Max} = 5 \cdot 10^{-3} \text{ A} \end{cases}$ .

3.  $u(t) = U_{Max} \cdot \sin(\omega t)$  and  $i(t) = I_{Max} \cdot \cos(\omega t)$  where  $\begin{cases} \omega = 1000 \text{ rd/s} \\ U_{Max} = 5 \text{ V} \\ I_{Max} = 10 \cdot 10^{-3} \text{ A} \end{cases}$ .

Exercise 3. RMS and average values (4 points)


Express  $u(t)$  for  $t \in [0; T]$  ( $T$  = period of the signal) before computing the average value and the RMS value of the following signal : (justify your answer)

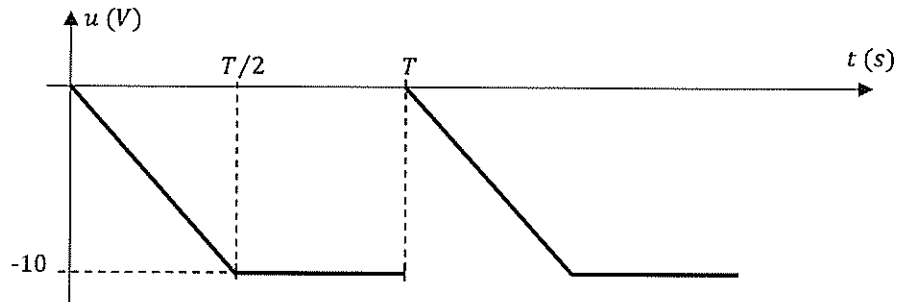

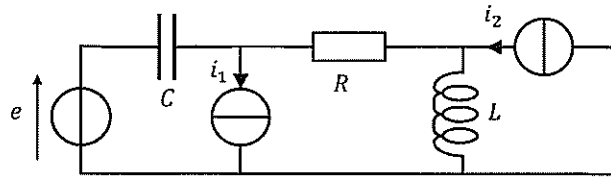Exercise 4. Sinusoidal regime (8 points)

We consider the following circuit :

$$\text{Where } \begin{cases} i_1(t) = I \cos(\omega t) \\ i_2(t) = I \sin(\omega t) \\ e(t) = E \sin(\omega t) \end{cases}$$



We assume that  $I, E, \omega, L, R$  and  $C$  are known.

1. Determine the complex amplitudes associated to  $i_1(t)$ ,  $i_2(t)$  and  $e(t)$ .

2. Express the current  $i(t)$  flowing through  $R$ .

*Rq : you have to start by representing this current on the circuit. Then, you can use the method that you want (superposition, Thevenin and/or Norton) in order to determine  $\underline{I}$ . If necessary, you can draw the equivalent diagram associated to each step in order to justify your answer (using the superposition theorem for example).*

